VCO

EURORACK DIY VCO MODULE

Feat:

Voltage controlled oscillator!

Uses a sawtooth core and waveshapes, folds, and flip-flops for a variety of different outputs

Fully hand solderable :0

It even has FM!

By Chris, 17
NZ